



Circuits Theory and Eletronic Fundamentals

Aerospace Engineering Master's Degree

Laboratory Report

Group 56

Alexandre Couto 95766

Bruno Pinto 95774

Hugo Aranha 95796

05/05/2021

Contents

1	Introduction	2
2	Circuit description	3
3	Circuit Analysis	4
4	Discussion of various tests and final results	5
5	Conclusion	7

1 Introduction

The objective of this laboratory assignment is to build an ac/dc converter using one ideal transformer and some diodes, resistors and capacitors. The challenge of this laboratory is to make the best ac/dc converter and for that we must be smart and make a balance quality vs cost, because the result will be the quotient between those quantities.

In this presentation, we will start to show an image of our ac/dc converter and explain why we choose that scheme. After that, we will present the ngspice simulations for this circuit and compare with octave theoretical analysis. Then we will go over some other configurations that were important to take some conclusions that were important to reach the final setup. To conclude, we will present some final conclusions.

2 Circuit description

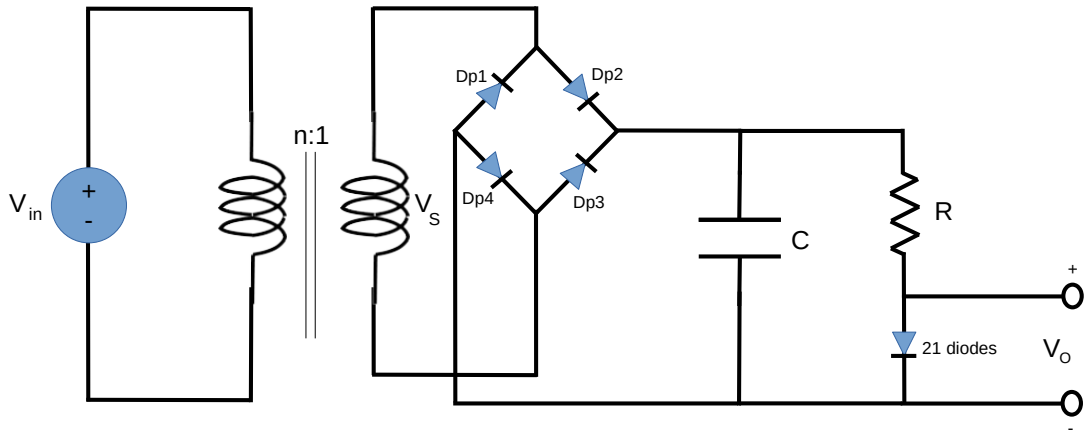


Figure 1: Circuit to be analysed in this report.

In this section, we will describe the circuit shown in Figure 1. In our configuration we use a transformer that has a ratio 15.54 : 1. Connected to the transformer, we use a full-wave bridge rectifier, using four diodes, and a capacitor connected in parallel with the rectifier. These two elements make the envelope detector. Then we connect in parallel with this circuit a series of 21 diodes and one resistor, consisting on a voltage regulator. In the following table we present the values to the the various components and parameters.

Name	Value [Ω or V or Hz or F]
Frequency	50.000000000000
Transformer n:1 ratio	15.54:1
Transformer amplitude	14.800000000000
R	12100.000000000000
C	0.000015000000
Diodes in voltage regulator	21

Table 1: Values of the various components and parameters

3 Circuit Analysis

In the following section we present the theoretical and simulation analysis, using Octave and Ngspice, respectively, comparing each other. To start with we will take a look at the voltage output, V_S , from the transformer. In both analysis the results obtained naturally don't differ, so we will just present one graph, in this case, produced by Octave.



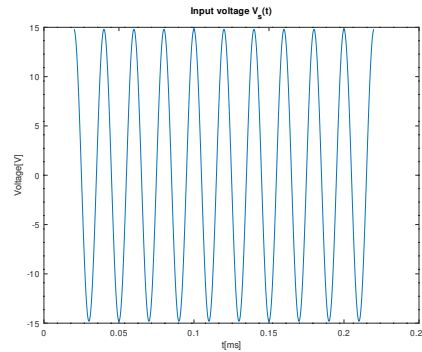


Figure 2: Results for V_S .

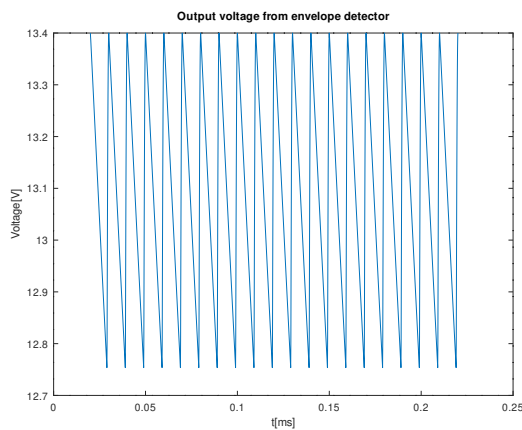Moving on to the output voltage from the envelope detector we can also expect not having the same results cause ngspice use complex methods and we are using the V_{ON} approximation. Despite that we can observe that the differences are small, meaning that the ideal diode model works "just fine".



(a)

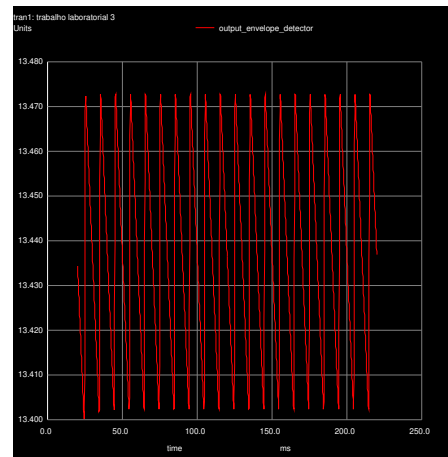

(b)

Figure 3: a) Voltage in envelope detector using octave b) Voltage in envelope detector using ngspice

In both plots we chose to neglect the first period since in ngspice in that time the circuit was not stable which would result in a bad calculation of the average values.

Lastly, we had to analyse the output voltage from the voltage regulator. In this last analysis we were also expecting some differences between both theoretical and simulation results, but in this case we expected lower differences due to the usage of a more accurate model which consists of solving non-linear equations using Newton-Raphson method.

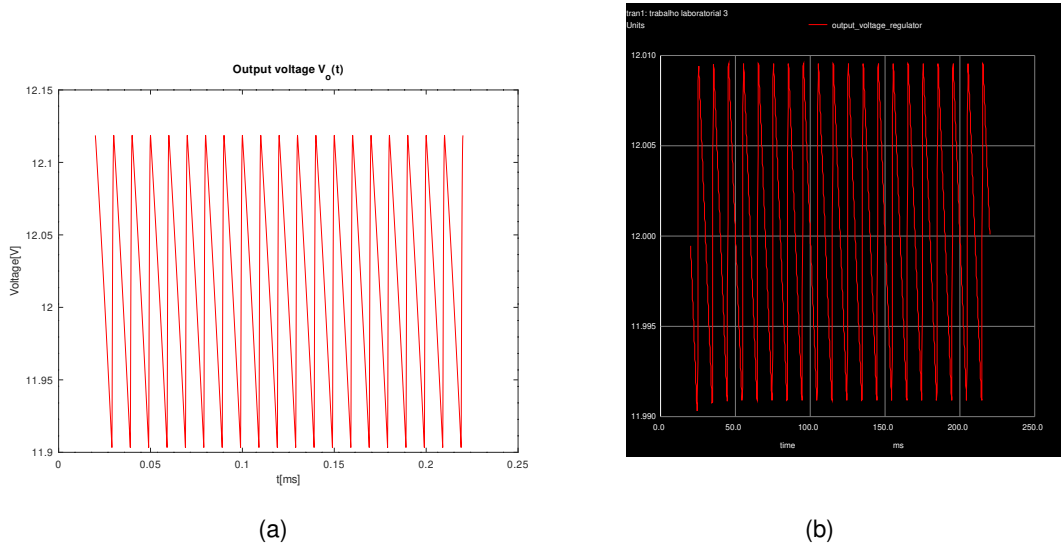


Figure 4: a) Voltage in voltage regulator using octave b) Voltage in voltage regulator using ngspice

4 Discussion of various tests and final results

In this section, we are going to discuss about some tests that were elaborated during the laboratory preparation which led to the final circuit (presented in the section 2). To compare the different configurations and to reach the best one we were based on the merit calculation. That is given by the formula:

$$M = \frac{1}{(cost \cdot (ripple(V_o) + average(V_o - 12) + 10^{-6}))} \quad (1)$$

Being the cost equal to the sum of the cost of the capacitor, diodes and resistors. The cost of the resistors equal to 1 monetary unit (MU) per Ohm, the cost of the diodes 0.1 MU per diode and the cost of the capacitor is 1 MU per μF .

By the formula it's crucial to not only have voltage output close to 12V and with low ripple, but also reduce as much as we can the cost.

Firstly, we tried to use an half-wave rectifier but we had to spend too much money on resistance and capacitance to reduce the high ripple due to the presence of only an half-wave rectifier, so from the start we had it clear that we needed to use a full-wave rectifier since the cost of three more diodes was definitely better than the waste on the other two components. Then we established the configuration presented in this assignment and the final one came from the alteration of the values of the resistance and capacitance and the number of diodes in the regulator.

So from all the configurations that were made we conclude that:

- High resistance and high capacitance lead to very low ripple and the average very close to 12V, but it was too expensive so we couldn't achieve a good merit;

- Low resistance and low capacitance are cheap in terms of the cost, but in terms of the output voltage there is too high ripple eventhough the average stays around 12V so the merit was not that good;
- If we spend a certain amount of money, the merit was not so good if we spend much more in resistance than in capacitance, and vice-versa. So we should not invest too much in only one of them;

After all the testing we can now look back at our best configuration and its results.

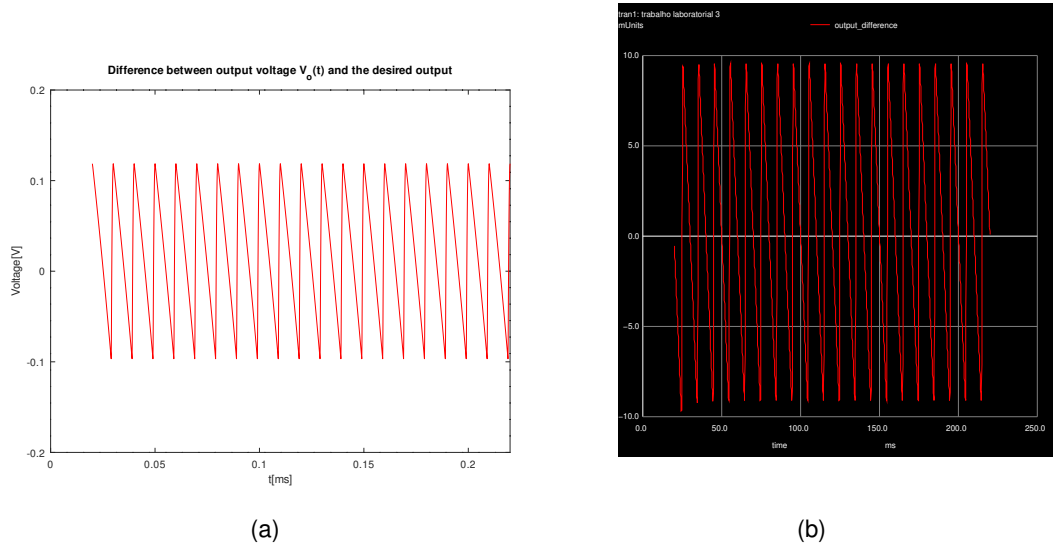


Figure 5: a)Deviation from 12V using octave b)Deviation from 12V using ngspice

As you can see in the graphs we have a small ripple and the average is close to 12V (can be seen in the nexts tables). Also they present similar results but for the reasons mentioned in section 2 (these plots are pretty closed to the previous ones, only deviated vertically from 12V).

The average values of the output are presented in the tables 2 and 3.

Name	Value [V]
Average	12.01810972321

Table 2: Average using Octave.

Name	Value [V]
average	1.200023e+01

Table 3: Average using Ngspice.

The ripple values of the output are presented in the tables 4 and 5.

Name	Value [V]
Max	12.11865071612
Min	11.90337594874
Ripple	0.21527476738

Table 4: Ripple using Octave.

Name	Value [V]
max	1.200954e+01
min	1.199031e+01
ripple	1.923000e-02

Table 5: Ripple using Ngspice.

The average and ripple values are close between each analysis which means that the methods used work good despite the differences.

In the next table we present the cost and the merit obtained using Ngspice.

Name	Value
cost	2.960000e+01
merit	1.735974e+00

Table 6: Cost and merit.

5 Conclusion

In the present laboratory we produced an AC/DC converter and analysed it successfully. In both theoretical and simulation analysis we achieved similar results even though there were non-linear components in it which we were expecting to bring bigger differences. As for merit obtained, after all the testing and research made we are happy with the result achieved at the end.

To approach a future work in this area we could study more components that can do the same job and who knows even be more efficient (like zener diodes or transistors).

So this laboratory contributed to our global knowledge and we think that it was important to absorb some concepts and skills for the course and who knows for a future job.